


---

# Ohm's Law for Closed Circuits


Senior High Physics · Electric Circuits

OPENING QUESTION

# Why does a battery heat up?

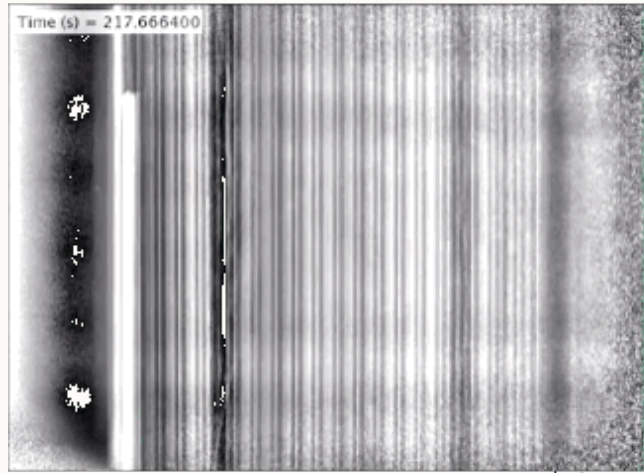

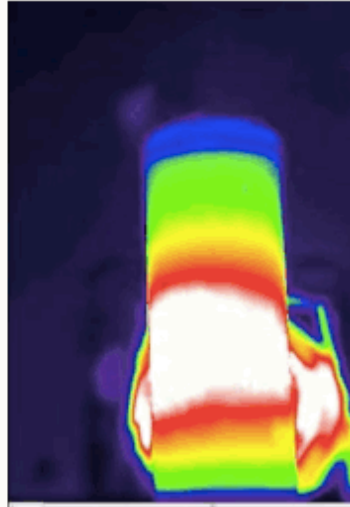Thermal image of an overheating lithium-ion battery




... sometimes with dramatic consequences

*And what is the expression for the heat it generates? Keep this question in mind — by the end of the lesson you will be able to answer it.*

## THE BIG PICTURE

# A closed circuit has two parts

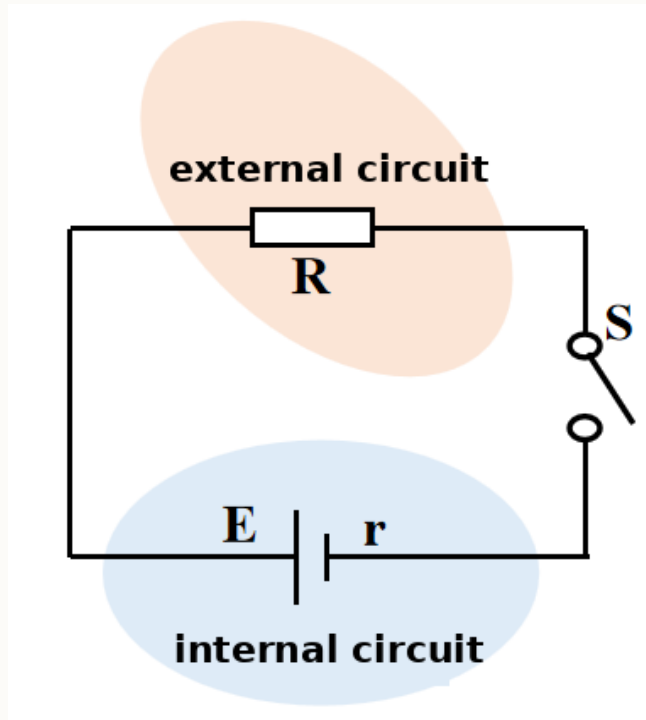

### EXTERNAL CIRCUIT


Everything outside the source: the resistance  $R$ , wires, switch — where the current does useful work.

### INTERNAL CIRCUIT

The inside of the source itself, with EMF  $E$  and internal resistance  $r$ .

*The current is the same everywhere in a series loop — including inside the battery.*

# What does the source actually do?

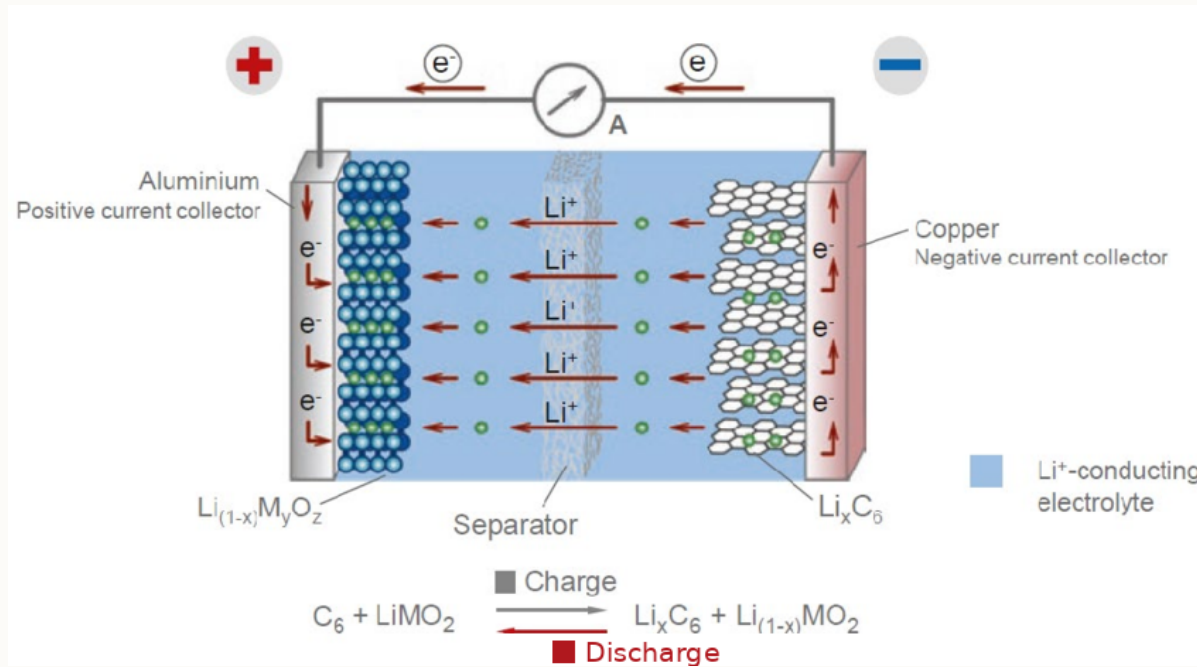

Ions and electrons on the move inside a lithium-ion cell during discharge

A source does not *create* charge. It **pumps** charge that is already there: positive charge is pushed from the low-potential terminal back up to the high-potential terminal, against the electric force.

*Something inside the source must be doing work on the charges. What is it?*

## NEW QUANTITY

# Electromotive force (EMF)

### PHYSICAL MEANING

Measures how strongly a source converts other forms of energy into electric potential energy.


### DEFINITION

The work done by non-electrostatic forces per unit charge moved through the source:

$$E = \frac{W}{q}$$
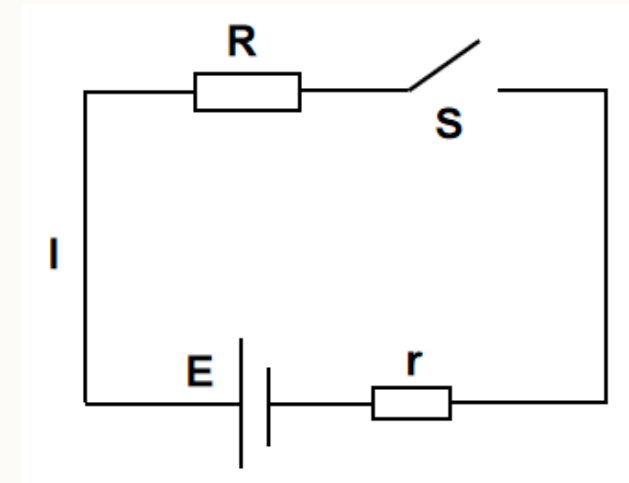
### UNIT

The volt (V) — the same unit as voltage, but *not* the same quantity.



A source of EMF  $E$  and internal resistance  $r$  driving a current


*A 1.5 V dry cell gives every coulomb of charge 1.5 J of energy as it passes through.*

## ANALOGY

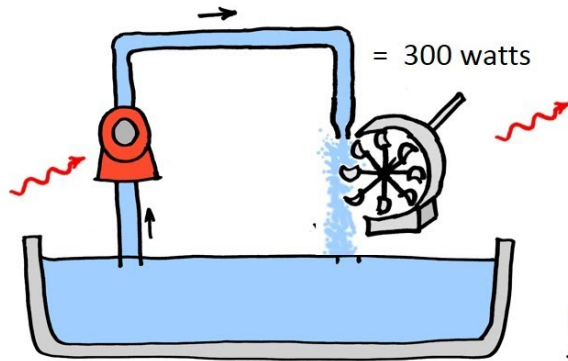
# EMF and voltage: the water model

$$\text{Power} = \text{Flow Rate} \times \text{Potential}$$

$$\begin{aligned} \text{Power} &= \text{Flow Rate} \times \text{Pressure} \\ &= 1 \text{ LPS} \times 300 \text{ kPa} \end{aligned}$$


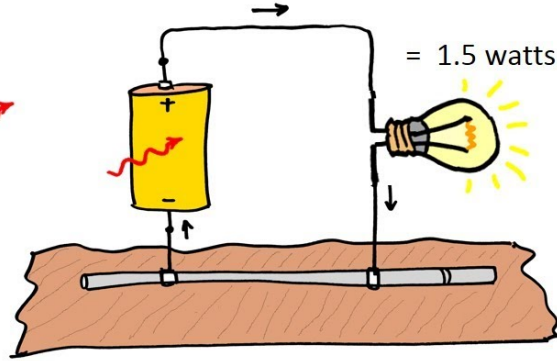
$$\begin{aligned} \text{Power} &= \text{Current} \times \text{Voltage} \\ &= 1 \text{ A} \times 1.5 \text{ V} \end{aligned}$$



The pump (source) lifts water; the waterwheel (resistor) extracts the energy

The **pump** raises water against gravity — like the source raising charge to a higher potential. The water flowing back down through the wheel is the current doing work in the external circuit.

*EMF describes the pump's lifting ability; voltage describes the drop across each part of the path.*

### EXAMPLE 1 • UNDERSTANDING EMF

Which of the following statements about EMF is correct?

- A The EMF of a source is proportional to the work done by non-electrostatic forces inside it, and inversely proportional to the charge that passes through
- B EMF has the same unit as voltage, so EMF is just the voltage between the two terminals of a source
- C The more work the non-electrostatic forces do, the greater the EMF
- D The EMF is determined by the nature of the non-electrostatic forces inside the source ✓

#### WHY

$E = W/q$  is a *defining* equation — it does not mean  $E \propto W$  or  $E \propto 1/q$  (A, C ✗). EMF corresponds to work done by *non-electrostatic* forces; voltage corresponds to work done by electrostatic forces, so they are different quantities even though the unit is the same (B ✗).

### EXAMPLE 2 · COMPARING TWO BATTERIES


A lead–acid battery has an EMF of 2 V; a dry cell, 1.5 V. Which of the following is correct?

- A The voltage between the terminals of the lead–acid battery is 2 V
- B The dry cell can convert 1.5 J of chemical energy into electrical energy in 1 s
- C The EMF of the lead–acid battery changes when it is connected to different circuits
- D For the same charge passing through, the non-electrostatic forces do more work in the lead–acid battery than in the dry cell ✓

#### WHY

Terminal voltage is generally *less* than the EMF once current flows (A ✗). 1.5 V means 1.5 J *per coulomb*, not per second (B ✗). EMF is a property of the source itself — it does not depend on the circuit (C ✗). From  $W = Eq$ , a larger EMF means more work for the same charge (D ✓).
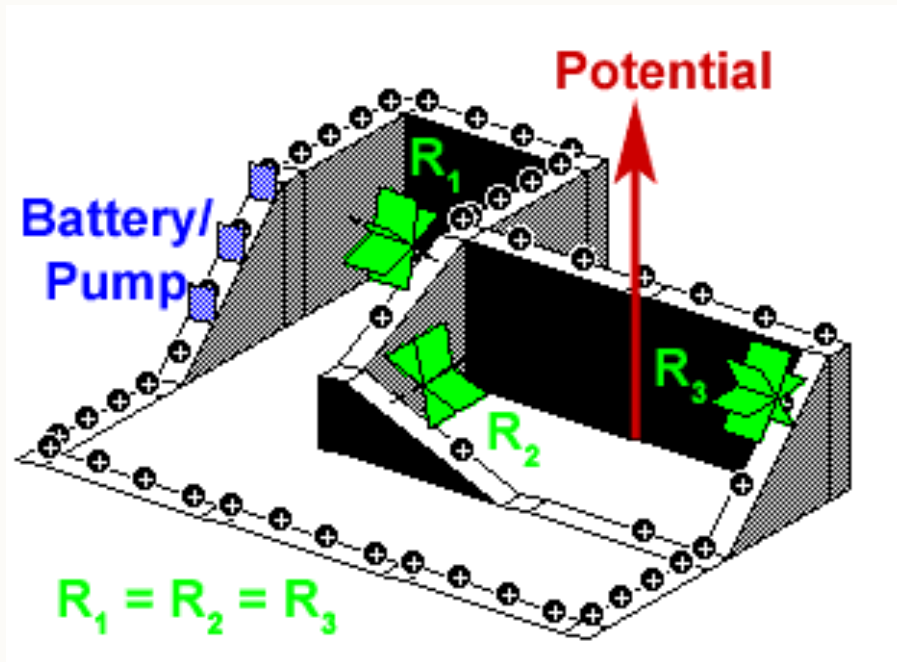
# How does the potential change around the loop?




Going around the external circuit, the potential **falls** step by step as the current passes each resistance.

Inside the source it must be **lifted back up** — otherwise the current could not keep flowing.

*The battery is the "staircase" of the circuit: everything that comes down must be carried back up.*

Potential around the circuit: a ramp down through the bulb, a sharp lift through the battery "pump"

# The non-electrostatic force

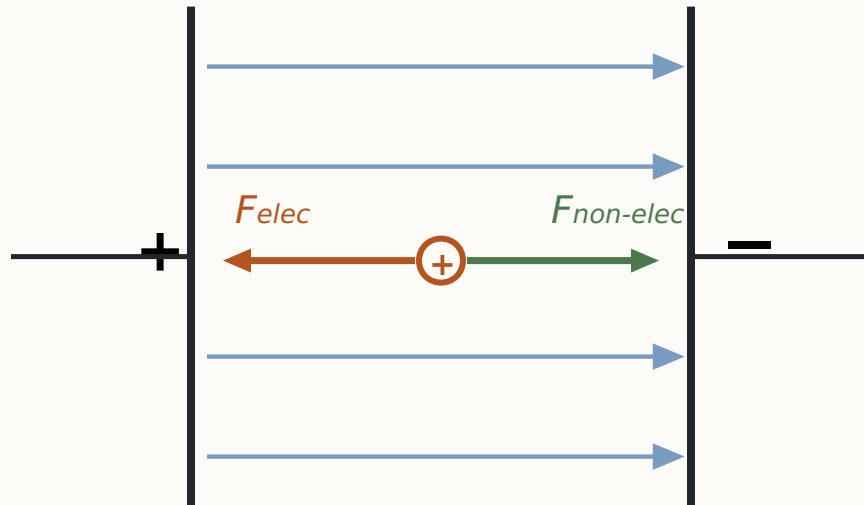

Inside the source, between the plates

Between the terminals the electric field pushes positive charge from + to - ( $F_{elec}$ ).

To move charge the *other* way, the source provides a **non-electrostatic force** ( $F_{non-elec}$ ) that does positive work on the charge, lifting its potential energy.

*In a chemical battery this force comes from chemical reactions; in a generator, from electromagnetic induction.*

ANALOGY

# The water carrier



Carrying water uphill takes work – and somebody has to pay the energy bill

*The carrier is the non-electrostatic force: he lifts the water (charge) back to the top against gravity (the electric force), spending his own energy (chemical energy) to do it.*

# Where the energy comes from



## CHEMICAL BATTERY

The non-electrostatic force is **chemical**: chemical energy → electric potential energy.



## GENERATOR

The non-electrostatic force is **electromagnetic**: mechanical energy → electric potential energy.

## SUMMARY

# EMF, in one box

$$E = \frac{W}{q}$$

EMF measures how strongly a source converts other forms of energy into electric potential energy. Its unit is the **volt**.

The value of  $E$  is decided by **the source itself** — it does not depend on the work  $W$ , on the charge  $q$  moved, or on the external circuit.

## CHECK YOURSELF

**Q1.** Which statement about EMF is correct?

- A** EMF is just voltage, and its unit is V
- B** A source with a larger EMF must do more work
- C** A source with a larger EMF must do work faster
- D** The EMF equals the energy the source supplies for each unit of charge passing through the circuit ✓

**Q2.** The EMF of a source reflects its ability to convert other forms of energy into electrical energy. Therefore —

- A** EMF is a kind of non-electrostatic force
- B** A larger EMF means the source stores more electrical energy
- C** The EMF reflects how much work the non-electrostatic forces can do per unit charge ✓
- D** EMF is the voltage across the source in a closed circuit

## PRACTICE

# Two batteries, two circuits

A lead–acid battery (EMF 2 V) and a dry cell (EMF 1.5 V) are connected to separate circuits, carrying currents of 0.1 A and 0.2 A respectively. Both circuits run for 20 s.

**How much chemical energy does each source consume? Which battery is better at converting chemical energy into electrical energy?**

### SOLUTION


$$W = EIt$$

$$\text{Lead–acid: } W_1 = 2 \text{ V} \times 0.1 \text{ A} \times 20 \text{ s} = 4 \text{ J} \quad | \quad \text{Dry cell: } W_2 = 1.5 \text{ V} \times 0.2 \text{ A} \times 20 \text{ s} = 6 \text{ J}$$

The dry cell converts *more total energy* here — but "converting ability" means energy *per unit charge*, which is exactly the EMF. Since 2 V > 1.5 V, the **lead–acid battery** is the stronger converter.

## MODELLING THE SOURCE

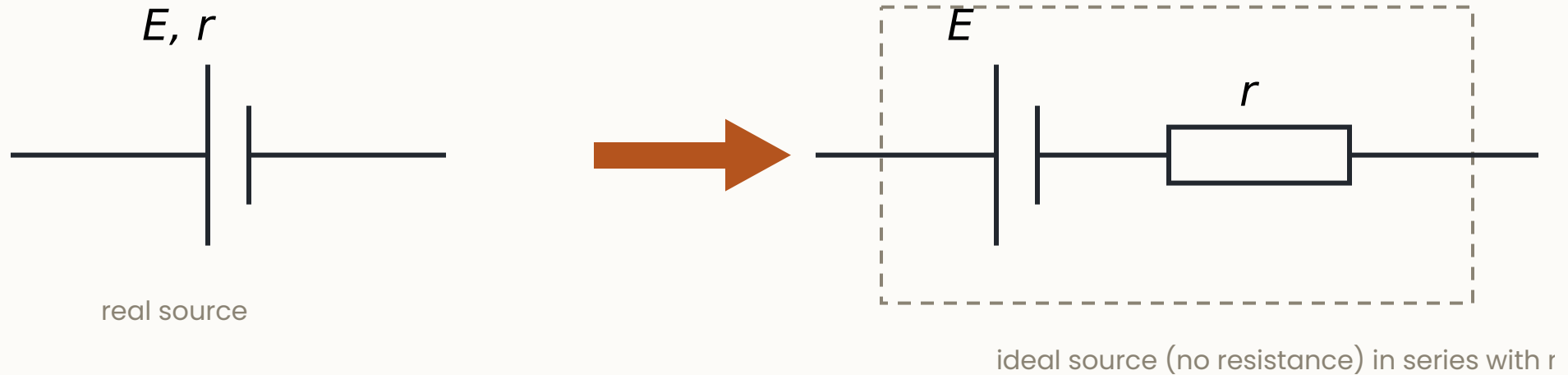
# A real source = ideal source + resistor



*Electrolytes and electrodes resist current too. We pull that resistance out of the battery symbol and draw it as an ordinary resistor  $r$  — the **internal resistance**.*

## KEY RELATIONSHIP

# Terminal voltage

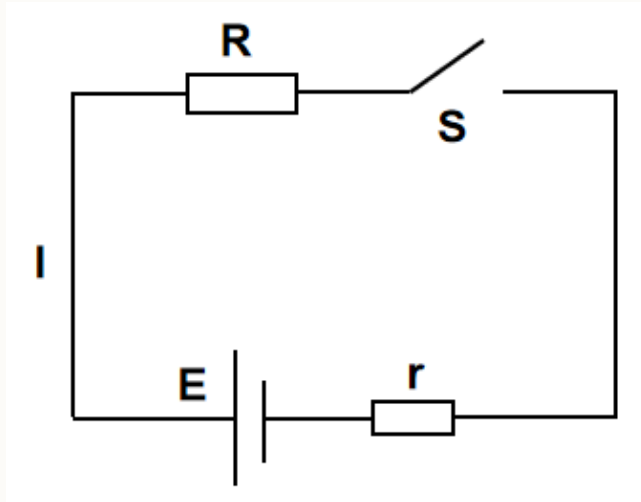

EMF  $E$ , internal resistance  $r$ , external resistance  $R$

Energy per unit charge from the source = energy dropped on  $R$  + energy dropped on  $r$ :

$$E = U_{ext} + Ir$$

so the voltage actually available at the terminals is


$$U_{ext} = E - Ir$$

$$I = \frac{E}{R + r}$$

*The larger the current, the more voltage is "lost" inside the source. With no current,  $U_{ext} = E$ .*
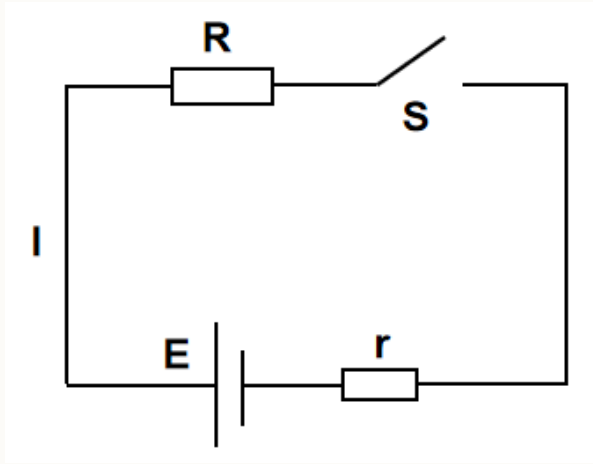
### EXAMPLE 3 · TERMINAL VOLTAGE

In the circuit shown,  $R = 2.0 \Omega$ , the EMF of the source is  $3.0 \text{ V}$  and its internal resistance is  $r = 1.0 \Omega$ . After switch  $S$  is closed, what is the terminal voltage?




#### SOLUTION

$$I = \frac{E}{R + r} = \frac{3.0 \text{ V}}{2.0 \Omega + 1.0 \Omega} = 1.0 \text{ A}$$

$$U = E - Ir = 3.0 \text{ V} - 1.0 \text{ A} \times 1.0 \Omega = \mathbf{2.0 \text{ V}}$$
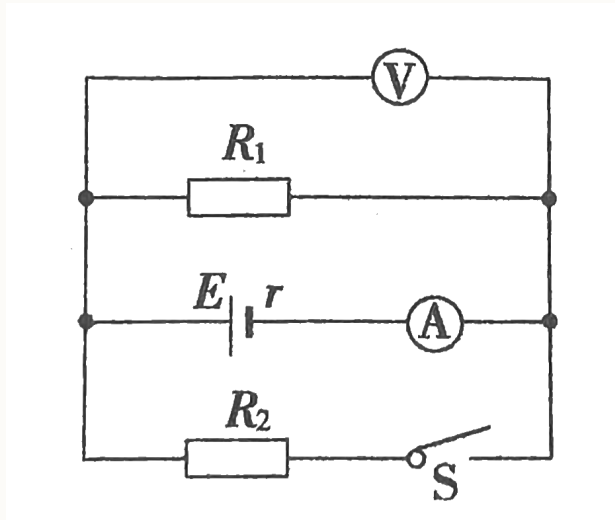
#### EXAMPLE 4 · FINDING E AND R FROM METER READINGS

When S is closed, the (ideal) voltmeter and ammeter read 1.6 V and 0.4 A. When S is opened, the readings change by 0.1 V and 0.1 A. Find the EMF and internal resistance of the source.



#### SOLUTION


Opening S removes the  $R_2$  branch, so the current falls and the terminal voltage rises: the two states are (1.6 V, 0.4 A) and (1.7 V, 0.3 A).

Apply  $E = U + Ir$  to both:

$$r = \frac{\Delta U}{\Delta I} = \frac{0.1 \text{ V}}{0.1 \text{ A}} = 1 \Omega \quad E = 1.6 \text{ V} + 0.4 \text{ A} \times 1 \Omega = 2.0 \text{ V}$$
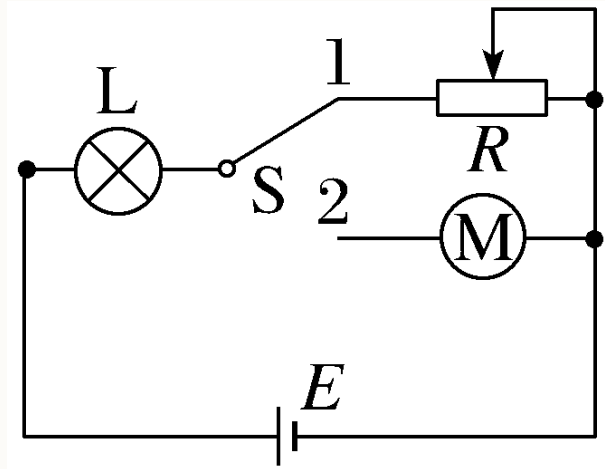
### EXAMPLE 5 · A CIRCUIT WITH A MOTOR

The source EMF is  $E = 6\text{ V}$ . Bulb L is rated "3 V, 0.9 W". With S at position 1 and the rheostat at  $R = 8\ \Omega$ , the bulb operates normally. With S at position 2, both the bulb and motor M work normally. The motor's coil resistance is  $R_0 = 2\ \Omega$ .



(1) Find the internal resistance of the source.

#### SOLUTION

$$\text{Normal operation: } R_L = \frac{U^2}{P} = \frac{(3\text{ V})^2}{0.9\text{ W}} = 10\ \Omega, \quad I = \frac{P}{U} = 0.3\text{ A}$$

$$E = I(R_L + r + R) \Rightarrow 6\text{ V} = 0.3\text{ A} \times (10\ \Omega + r + 8\ \Omega) \Rightarrow r = 2\ \Omega$$

**EXAMPLE 5 · CONTINUED**

(2) Find the motor's input power, output power and efficiency.

**SOLUTION**

With S at 2 the bulb still works normally, so the current is unchanged:  $I = 0.3 \text{ A}$ . The motor's operating voltage:


$$U_M = E - I(R_L + r) = 6 \text{ V} - 0.3 \text{ A} \times 12 \Omega = 2.4 \text{ V}$$

QUANTITY	RELATION	VALUE
Input power	$P_{in} = U_M I$	<b>0.72 W</b>
Heating power	$P_{heat} = I^2 R_0$	0.18 W
Output power	$P_{out} = P_{in} - P_{heat}$	<b>0.54 W</b>
Efficiency	$\eta = P_{out} / P_{in}$	<b>75%</b>

*A motor is not a pure resistor — Ohm's law applies to its coil resistance only, not to the motor as a whole.*

## APPLICATION

# The ohmmeter

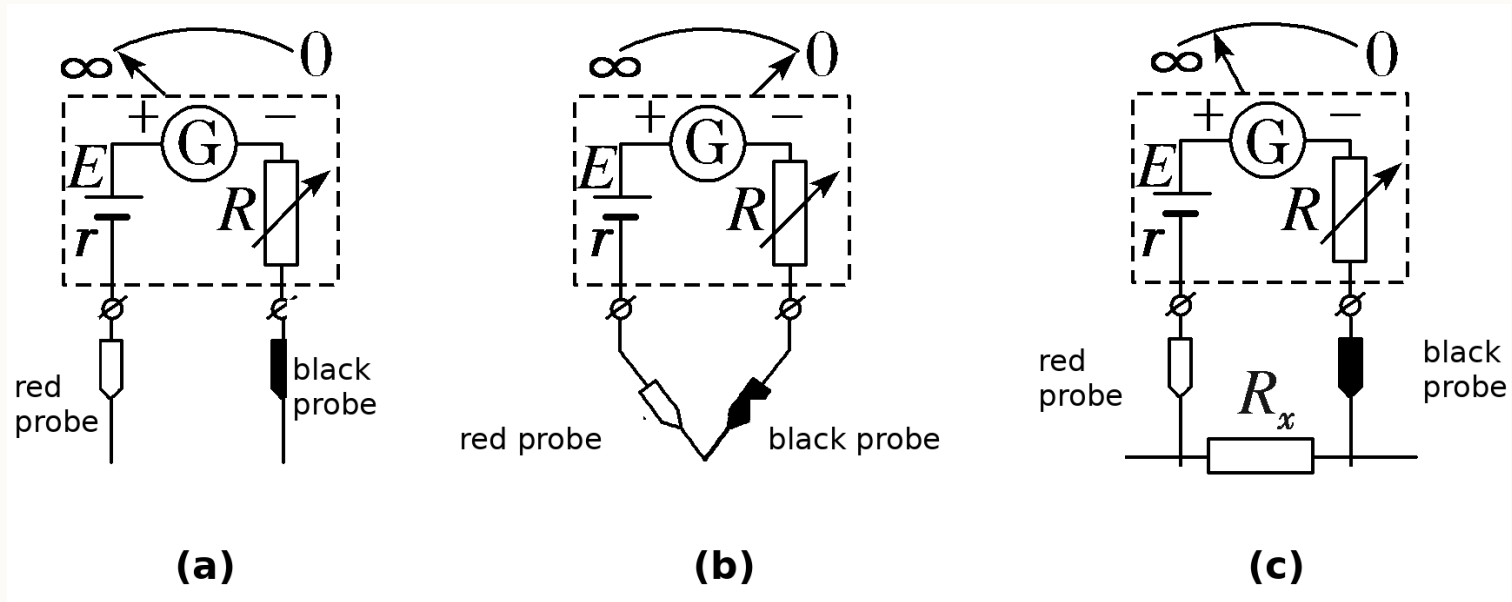

*A battery ( $E, r$ ), a galvanometer  $G$  and an adjustable resistor  $R$  in series — the measuring principle is exactly **Ohm's law for closed circuits**: a known EMF drives a current that depends on the unknown resistance.*

# From current to resistance

With an unknown  $R_x$  across the probes:

$$I = \frac{E}{R + R_g + r + R_x} \implies R_x = \frac{E}{I} - (R + R_g + r)$$

Each  $R_x$  gives exactly one current  $I$  — so relabel the current scale with resistance values and read  $R_x$  directly.

**Internal resistance:**  $R_{int} = R + R_g + r$


**Zero adjustment:** touch the probes, tune R until the pointer reads full scale ("0  $\Omega$ ").

MARK	CONDITION	POSITION
"0 $\Omega$ "	probes together, full deflection	far right ( $I_g$ )
" $\infty$ "	probes apart, no deflection	far left ( $I = 0$ )
<b>mid-scale</b>	$R_x = R_{int}$	centre of dial

*The scale runs "backwards" ( $\infty$  on the left) and is non-uniform — most cramped at the high-resistance end.*

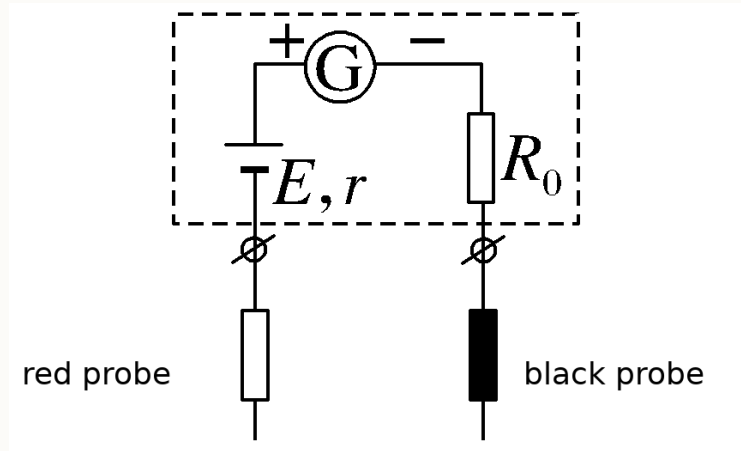**WORKED EXAMPLE · OHMMETER SCALE**

The meter's full-scale current is  $I_g = 500 \mu\text{A}$ ; the dry cell's EMF is 1.5 V. Fill in the resistance value for each current mark.



**SOLUTION**

Zeroing (probes together, full scale):  $R_{int} = \frac{E}{I_g} = \frac{1.5 \text{ V}}{500 \mu\text{A}} = 3\,000 \Omega$

Measuring:  $R_x = \frac{E}{I} - R_{int}$

<b>CURRENT MARK</b>	0	200 $\mu\text{A}$	300 $\mu\text{A}$	500 $\mu\text{A}$
<b>RESISTANCE MARK</b>	$\infty$	$4.5 \times 10^3 \Omega$	$2 \times 10^3 \Omega$	0

### WORKED EXAMPLE · CONTINUED

(2) What is the total internal resistance of this ohmmeter? When the pointer deflects to  $\frac{1}{3}$  of full scale, what is the resistance being measured?

#### SOLUTION

From part (1), the total internal resistance is **3 000  $\Omega$** .

$$\text{At } \frac{1}{3} \text{ of full scale: } I = \frac{I_g}{3} = \frac{500 \mu\text{A}}{3}$$

$$R_x = \frac{E}{I} - R_{int} = 3 \times 3\,000 \Omega - 3\,000 \Omega = \mathbf{6\,000 \Omega}$$

*Handy rule: at  $1/n$  of full scale,  $R_x = (n - 1) \cdot R_{int}$ .*

---

$$E = U_{\text{ext}} + Ir$$

One equation, the whole lesson: the source gives every unit of charge an energy  $E$ ; part is delivered outside, part is lost inside. And the battery heats up because of that inside part — at a rate  $P = I^2r$ .